

06/05/2020.

BEC - ASSIGNMENT - 3C3 :-

Anirudh Jakhotia


S20190010007

Q1) Astable Multivibrator using 555 timer :-


The 555-timer IC can be used with a few simple components to build an astable circuit which provides a 'square wave'. This is a digital wave, formed with sharp transitions between low (0V) and high (7V). The durations of the low and high states may be different. The circuit is called astable because it is not stable in any state.

555-timer

→ the output is continuously changing between 'low' and 'high'.

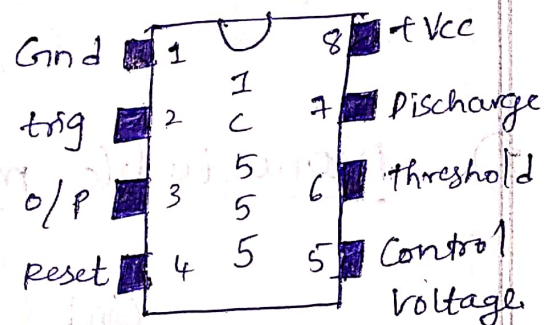Astable multivibrator

$$R_B = R_1 + V_{R_1}$$

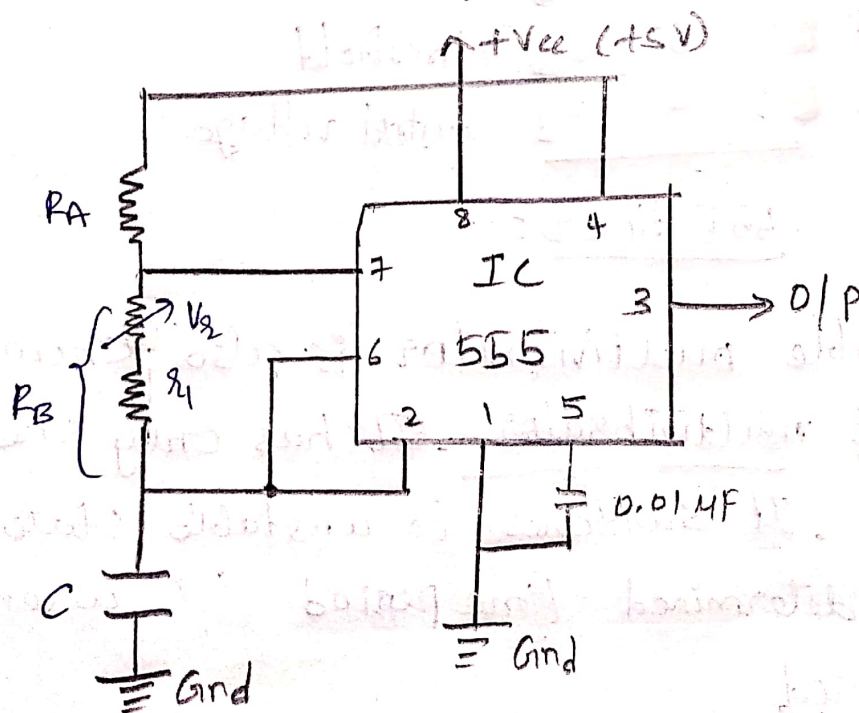

Expression for time period :-

$$T = t_c + t_d$$


$$\begin{cases} t_c = 0.69 (R_A + R_B) C \\ t_d = 0.69 (R_B C) \end{cases}$$

$$\boxed{T = 0.69 (R_A + 2R_B) C}$$


Frequency f

$$f = \frac{1}{T}$$

$$f = \frac{1}{0.69 (R_A + 2R_B) C}$$

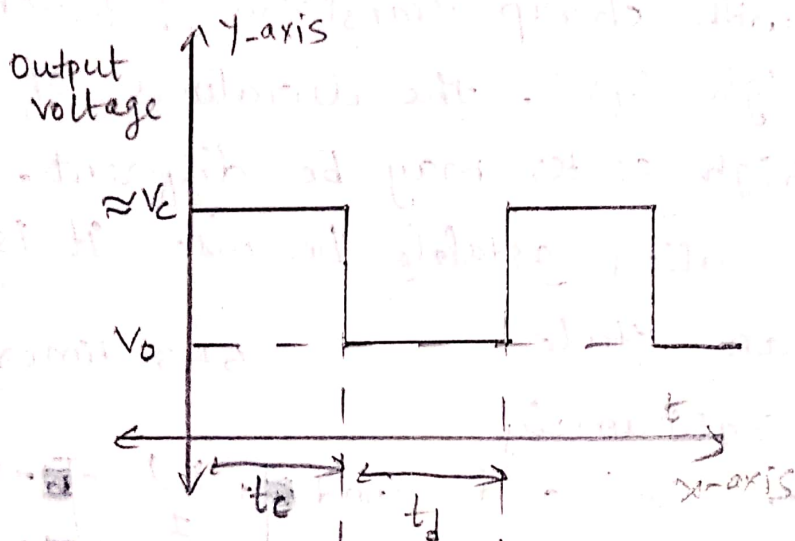

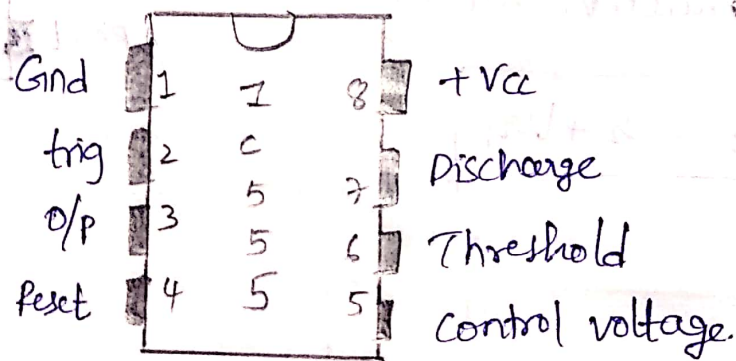2) Monostable multivibrator using 555 timer :-




555 timer :-

Monostable multivibrator is also known as one shot multivibrator. It has only one stable state. It switches to unstable state for a predetermined time period 'T' when it is triggered.

- ⇒ The time period 'T' is determined by RC time constant in the circuit.
- ⇒ Monostable state or mode of 555 timer is commonly used for generating pulse width modulation (PWM) waves.

Monostable multivibrator:-

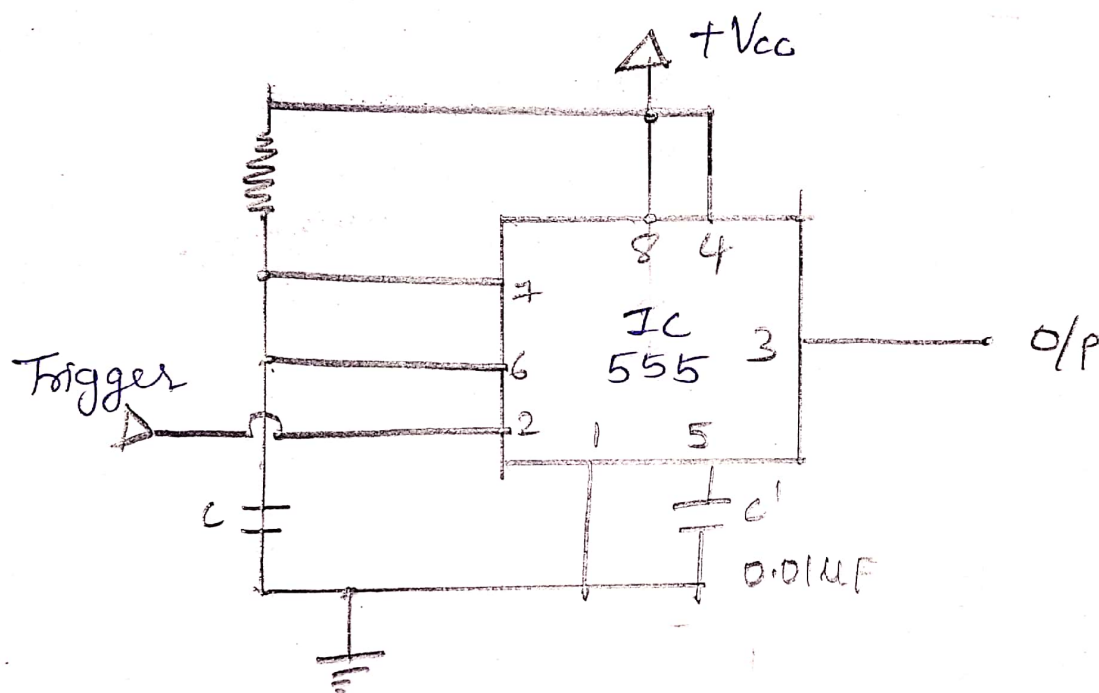

We know that the voltage across the capacitor 'C' rises exponentially. Hence, the equation for the capacitor voltage V_C can be written as

$$V_C = V_{CC} (1 - e^{-t/RC}) \quad \left[\text{When capacitor voltage is } \frac{2}{3} V_{CC} \right]$$

$$\frac{2}{3} V_{CC} = V_{CC} (1 - e^{-t/RC})$$

$$e^{-t/RC} = \frac{1}{3}$$

$$-\frac{t}{RC} = \ln\left(\frac{1}{3}\right)$$

$$-\frac{t}{RC} = -1.098$$

$$t = 1.098 RC$$

$$[t \cong 1.1 RC]$$