

## BEC : (Basic electronic circuits)


Basic electrical quantities :-

- 1) current
- 2) voltage
- 3) power

Electricity is a flow of electric charges.  
Current is the rate of flow of electrons (unit ampere).  
Unit is Ampere (A)

$$I = \frac{Q}{t} = \frac{\text{charge}}{\text{time}}$$

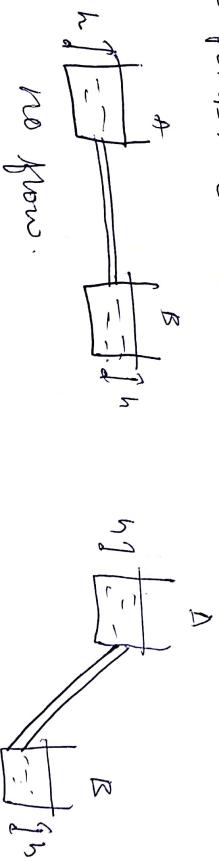Voltage (or Potential difference) :- It is the electrical force that would drive an electric current between two points. Unit is Volt (V)



no flow.

height difference - potential drift  
water - electrons (electric current)  
flow of water

Circuit :- A voltage source (battery) has two terminals that has a difference in electric potential. When there is a closed path between these two terminals, it is called a circuit.


In the absence of a circuit, current will not flow, if there is a voltage.

Terminal: It is a point where electrical connection can be made.

Circuit elements:

Passive elements (will not be able to amplify power)

Resistor ( $R$ )  ( $\Omega$ )

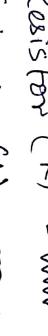Inductor ( $L$ )  (Henry)

Capacitor ( $C$ )  (Faraday)

Variable elements

Resistor ( $R$ ) 

Inductor ( $L$ ) 

Capacitor 

Resistor: Electrical component that opposes the flow

of electric current

Q. What is material used for making resistor? (Carbon material with metal oxide)

→ Power is dissipated in resistor in form of heat

⇒ Inductor: It is also called coil, choke, reactor.

elect compn.  
It is a passive two terminal that stores energy in magnetic field.

Capacitor: It is a passive two terminal electrical component that stores energy in electrical field.

Active elements:

Transistor is an example for an active element that can amplify power.

But sound is amplified in an amplifier

E

→ Sources are of two categories:

Independent sources:

① Voltage source  $\frac{1}{T}^+$  (Polarity).

- A two terminal device which can maintain a constant voltage.

② Current source  $I \uparrow$ .

An electronic circuit that delivers constant current to the load.


Various voltage / current wave forms:

$\frac{V_c}{t}$  AC Standard Indian electric supply

220V, 50Hz

AC voltage source American electric supply

120V, 60Hz

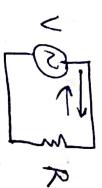

Dependent sources:

- 1) Voltage source whose magnitude is dependent on voltage of another current elsewhere in circuit.



2)

Dependent current source:

Current source whose magnitude is dependent on voltage or current elsewhere in a circuit.

Dependent current source

$$\begin{array}{ll} V_C & V_S \\ C & V_S \\ V_C & C_S \\ C & C_S \end{array}$$

-  
Ohm's law! 
$$V = IR$$

The current through a conductor between two points is directly proportional to the voltage across the points.

Series and parallel circuits:

In a series circuit, voltage divides proportionally to resistance value and the current flowing through the elements is same.

$$\text{Given } V = \frac{V}{R_1 + R_2 + R_3} = \frac{V}{6}$$

$$I = \frac{V}{R_1 + R_2 + R_3} = \frac{V}{6}$$

$$R_3 = 3\Omega$$

$$R_{\text{eff}} = R_1 + R_2 + \dots + R_n$$

$$V_{R_1} = IR_1 = \frac{V}{6}$$

$$V_{R_2} = IR_2 = \frac{V}{3}$$

$$V_{R_3} = IR_3 = \frac{V}{2}$$

In a parallel circuit, voltage remains the same and the current divides in inverse relation to that of resistor.



$$I_1 = \frac{V}{R_1} = \frac{6}{2} = 3A$$

$$I_2 = \frac{V}{R_2} = \frac{6}{3} = 2A$$

$$I_3 = \frac{V}{R_3} = \frac{6}{6} = 1A$$

$$V = IR = 1A \times \frac{6}{2} = 6V$$

$$\frac{1}{R_{\text{eff}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

### Equivalent Resistance

$$\text{Series resistors: } R_{\text{eq}} = R_1 + R_2 + R_3 + \dots$$


$$\text{Parallel resistors: } \frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

$$\text{Given } \frac{1}{R_{\text{eq}}} = \frac{1}{100\Omega} + \frac{1}{200\Omega} = \frac{1}{100\Omega}$$


$$R_{\text{eq}} = 100\Omega$$

2) 

$$R_{eq} = \frac{100 \times 10}{10+100} \Omega = 9.09 \Omega$$

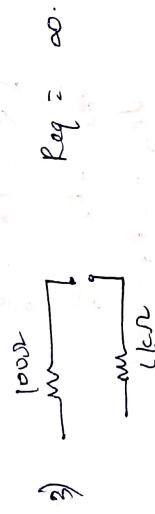3) 

$$R_{eq} = \infty$$

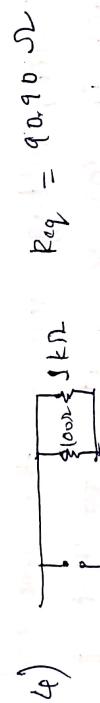4) 

$$R_{eq} = 90.9 \Omega$$

5) 

$$R_{eq} = 1 \Omega$$

→ Power generated and Dissipated in the Circuit!

power generated by voltage source  $P = IV$ .  
 power dissipated in resistor  $R_1$   $P = I^2 R_1 = \frac{V^2}{R_1}$

1) 

$$P = \frac{V^2}{R_{eff}}$$

$$\frac{1}{R_{eff}} = \frac{1}{R_1} + \frac{1}{R_2}$$

2) 

$$V = 18$$

$$I = 7A$$

$$I_1 = 3A$$

$$I_2 = 4A$$

$$R_{eff} = \frac{V}{I} = \frac{25}{7} \Omega$$

$$\frac{1}{R_{eff}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{25} = \frac{1}{1} + \frac{1}{18}$$

$$R_{eff} = 1.8 \Omega$$

$$V_x = 25V$$

$V = 18$   $I = 7A$   $I_1 = 3A$   $I_2 = ?$

$I = I_1 + I_2$   
 $I = 3 + I_2$   
 $I_2 = 4$

$\boxed{I_2 = 4}$

## Semi-conductor devices:-

Materials can be classified into three categories based on conductivity (σ) & resistivity (ρ).


① Conductors  $(\rho) < 10^3 \Omega^{-1}\text{cm}^{-1}$   
② Semi-conductors  $\text{Silicon at room temp.} = 2.31 \times 10^5 \Omega^{-1}\text{cm}^{-1}$   
③ Insulators  $(\rho) > 10^8 \Omega^{-1}\text{cm}^{-1}$ .

## Intrinsic semi-conductors:-

Semi-conductors in its pure form is called as intrinsic semi-conductors.
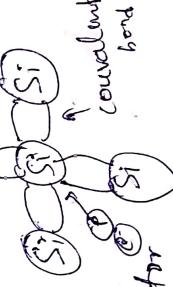
## Extrinsic semi-conductors:-

Pure semi-conductor added with dopant impurity.



## Intrinsic carrier concn:-

No. of  $e^-$  or holes in a semi-conductor at room temp.  $n_i$  Intrinsic carrier concn. of silicon at room temp  $1.45 \times 10^{16} \text{ cm}^{-3} = n_i$

In, Intrinsic semi-conductor at thermal equilibrium

$$n_0 p_0 = n_i^2$$

$n_0 = \text{electron carrier concn at room temp}$   
 $p_0 = \text{hole carrier concn at room temp}$

$$n_0 + p_0 = N_p \rightarrow 10^{15} / \text{cm}^3$$

$$n_0 = 1.45 \times 10^{10}$$

$$p_0 = 1.45 \times 10^{10}$$

$$n_0 + p_0 \rightarrow 10^{15}$$

## Calculations of e<sup>-</sup> and hole concn in a doped

→ Donor doped (Phosphorus) ND

The e<sup>-</sup> concentration in a donor doped semi-conductor

$$n_s = n_D \approx N_D$$

where N<sub>D</sub> is donor doping concentration.

$$\rightarrow \text{the whole concn is } P_0 = \frac{n_i^2}{n_0 + n_D} = \frac{n_i^2}{n_D}$$

Q) Calculate e<sup>-</sup> and hole concentrations in a silicon doped with donor concn (P) of  $10^{16} \text{ cm}^{-3}$ .

$$\text{Sol: } P_0 = \frac{(1.45 \times 10^{16})^2}{10^6} = 2.10 \times 10^{20-16} = 2.10 \times 10^4$$

$$n_0 (2.10 \times 10^4) = (1.45 \times 10^{16})^2$$

$$e^+ = n_0 + p = \frac{n_0}{2.10 \times 10^4} = \frac{2.10 \times 10^{20}}{2.10 \times 10^4} \approx N_D = 10^{16}$$

With donor impurity (I)

If intrinsic silicon is doped with donor impurity (I), e<sup>-</sup> are majority carriers and holes are the minority carriers. (n-type material)

If intrinsic silicon is doped with donor impurity (D)

→ If intrinsic silicon is doped with donor impurity (D), e<sup>-</sup> are minority carriers and holes are majority carriers (p-type material)




### Kirchoff's Current Law:

Alg. Sum of all the currents through a point is zero.
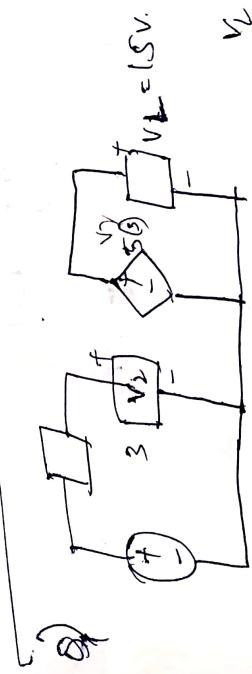
### Kirchoff's Voltage Law:

Alg. Sum of voltages in a closed loop is zero.



$$V_2 = 3V$$


$$V_L = 5V$$

$$V_L - 5V_2 = 0$$

$$V_L = 5V_2$$

$$\begin{aligned} V_L &= 5V_2 \\ V_L &= 5 \times 3 \\ V_L &= 15V \end{aligned}$$


find power absorbed  
by each element.

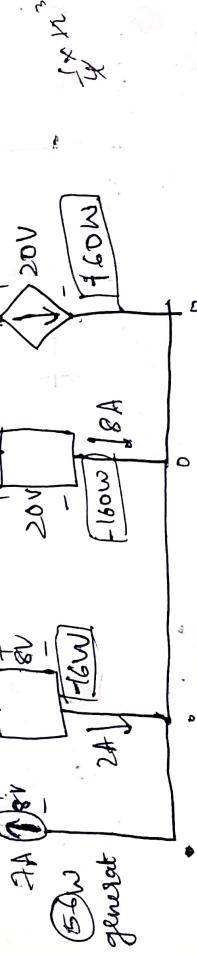

find power absorbed  
by each element.

5Ω genet



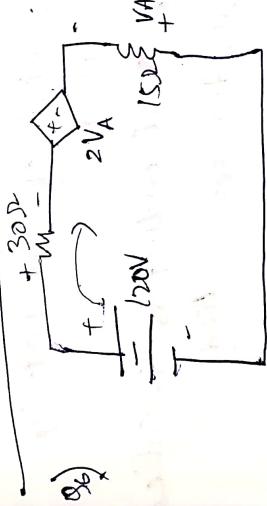

11

Compute power absorbed in each element

$$i = \frac{VA}{R}$$

$$120^\circ - 30^\circ - 20^\circ + V_A = 0 \quad \Rightarrow \quad V_A = \frac{80}{3}^\circ$$

$$120x = 451$$

$$204 - 301 = 151$$


$$T = \text{Col}^M$$

$$P = \frac{640}{3}$$

$$V_A = \frac{1}{2} B^2 \frac{L^2}{\rho}$$

1

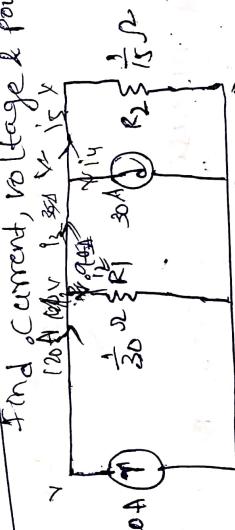Find current, voltage & power associated with each element



$$e^{\frac{1}{kT}} = \frac{1}{\sigma}$$

$$m_0 = \frac{1}{3} \Omega$$

23/01/2020

## Rectification - (AC - DC):

P is n-type  
 mobile / majority -  $\rightarrow$   
 minority - holes

I = conventional current.

Forward bias:


$\frac{I}{I_n}$  when (+) terminal of the battery is connected to P region, (-) terminal of the battery is connected to n-region.

This combination of semi-conductors is called diode.

$$I_h = \text{hole current} \\ I_c = e \text{ current}$$


Reverse bias:

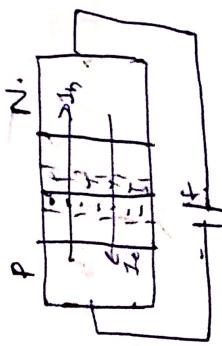- terminal of p region + terminal of n region




$$V_I = 0, V < 0 \Rightarrow V \\ V > 0, V \geq 0.7V$$

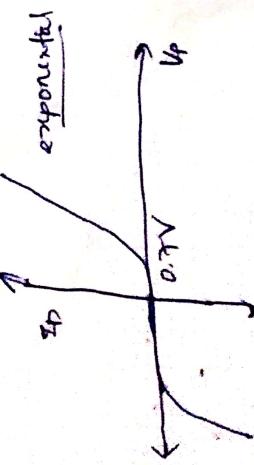
V length of depletion layer increases exponentially



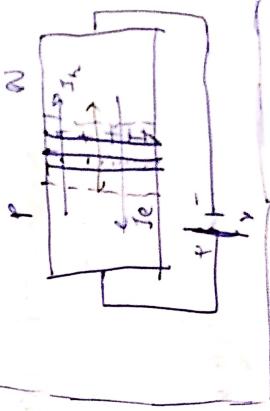Silicon Built-in-potential  
 $V_T = 0.7V$



### Half-wave Rectifier

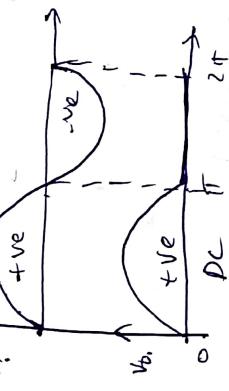

$$V_{avg} = \frac{1}{2\pi} \int_0^{\pi} V_m \sin \theta d\theta$$

$$= \frac{V_m}{2\pi} - (\cos \theta)_0^{\pi} = \frac{-V_m}{2\pi} (-1-1) = \frac{V_m}{\pi} // \text{ using } \int \cos \theta d\theta = \sin \theta$$

$$\boxed{V_{avg} = \frac{V_m}{\pi}}$$

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{\pi} (V_m \sin \theta)^2 d\theta}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \int_0^{\pi} \left(1 - \frac{\cos 2\theta}{2}\right) d\theta}$$

$$= \sqrt{\frac{V_m^2}{4\pi} \left[ \theta - \left(\frac{1-\cos 2\theta}{2}\right) \right]_0^{\pi}} = \sqrt{\frac{V_m^2}{4}}$$

$$\boxed{V_{rms} = \frac{V_m}{2}}$$

$$\text{Efficiency} = \frac{V_{avg}}{V_{rms}} = \frac{V_m'}{\frac{V_m}{\pi}} = \frac{2}{\pi} \approx 66.7\%$$

$$\boxed{I_D = I_s e^{\frac{V_D}{V_T}} \text{ (approx.)}}$$

$I_D$  = Saturation current  
 $I_s$  = saturation current  
 $V_D$  = Voltage across diode  
 $V_T$  = Thermal voltage  
 $= 26 \text{ mV (at room temp)}$

$$\theta \approx \frac{V_D}{V_T}$$


Q) Find out the average and rms voltages of Indian supply voltage fed to a half-wave rectifier.

$$\text{Sol: } V_{\text{avg}} = \frac{V_m}{\pi} \quad V_{\text{rms}} = \frac{V_m}{2}$$

$$V = \frac{220\sqrt{2} \sin(2\pi 50t)}{V_m} \quad \omega = 2\pi f = 100 \quad V_{\text{rms}} = \frac{110}{2} = 55.50V.$$


$$V_{\text{avg}} = \frac{220\sqrt{2}}{\pi} = 98.98V$$

24/01/2020 Full-wave Rectifier

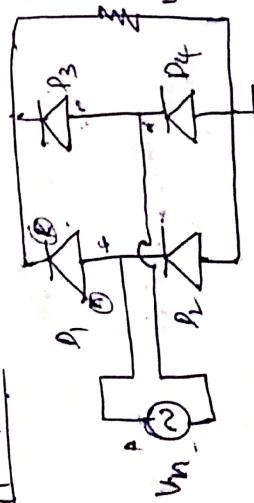



During the half cycle

D\_1 ON D\_3 OFF  
D\_2 OFF D\_4 ON.

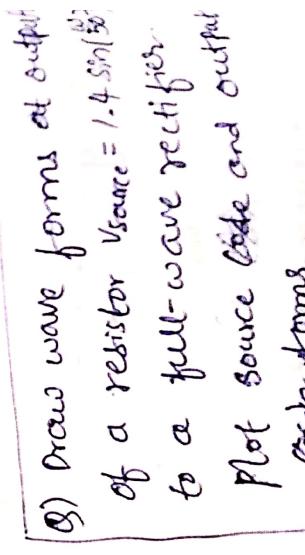

Q) Draw wave forms at output of a resistor  $V_{\text{source}} = 1.4 \sin(100t)$  fed to a full-wave rectifier.  
Plot source side and output side wave forms.  
Assume potential drop in each diode is 0.7V.

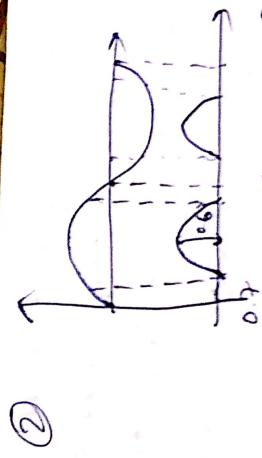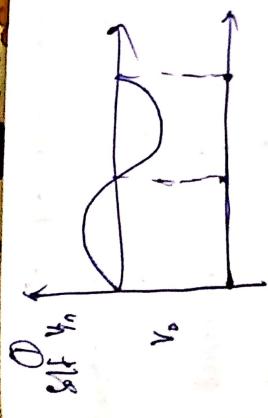During the half cycle  
D\_1 OFF D\_3 ON  
D\_2 ON D\_4 OFF



$$V_{avg} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \theta d\theta$$


$$= \frac{V_m}{\pi} - (\cos \theta)_0 \Big|_0^\pi = \frac{V_m(2)}{\pi} = \frac{2V_m}{\pi}$$

$$V_{rms} = \sqrt{2} \times \frac{V_m}{2} = \frac{V_m}{\sqrt{2}}$$

$$df \quad V_{average} = 2 \sin \omega t$$
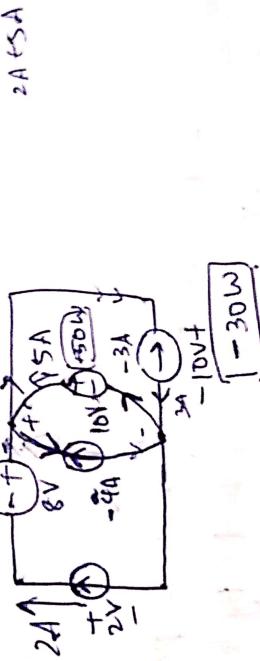
### Problem ①

Determine power delivered by each element on Circuit.



$$2V + 8V$$

- ⑦ Same current flows through each element. The voltage-controlled dependent source provides a current which is 5 times as large as the voltage  $V_x$ .

- (a) for  $V_x = 10V$  and  $V_x = 2V$ , determine power absorbed by each element (b) Is element A likely a passive or active source? Explain

(c)



$$\text{For } V_x = 2 \times 10 = 20W$$

$$\text{For } V_x = 10(10) = -100W \text{ (passive)}$$

$$\text{For } V_x = 8(10) = 80W$$

$$\text{For } V_x = 10 + 8 = 18W$$

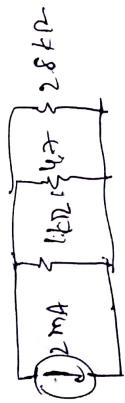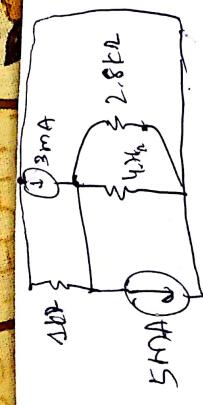- ⑧ Circuit below is in fact a single-node-pair circuit.
- (a) Determine the power absorbed by each resistor.  
 (b) Determine the power supplied by each current source  
 (c) Show that the sum of the absorbed power calculated in (a) is equal to sum of the supplied power calculated in (b).
-



$$R_2 = \frac{1}{I} + \frac{1}{4\Omega} + \frac{1}{2.8}$$

$$\frac{1}{R} = 1 + 0.35 + 0.2$$

$$\frac{1}{R} = 1.56$$

$$R = 0.64\Omega$$

$$V = I R$$

$$V = 2 \times 10^3 \times 0.64 \times 10^{-3}$$

$$V = 1.28 V$$

28 [01] 1000


DC Power Supply:


Transformers (Bring down high voltages to low voltage without change of frequency)

→ A device that

$P_{ac} = V I \cos \phi$ . Transformer  $\frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{I_2}{I_1}$  Primary  $\frac{N_1}{N_2}$  & secondary  $\frac{V_1}{V_2}$  winding


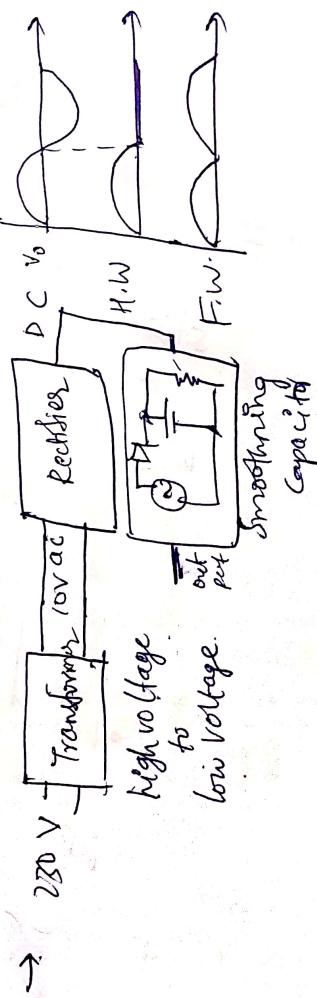
→ If the turn ratio is 1, then it PS  
Isolation transformer



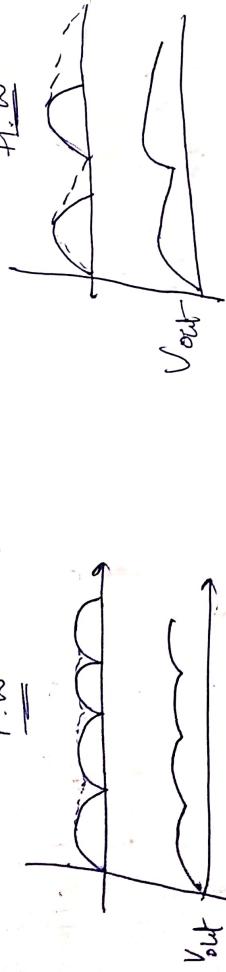

To avoid low voltage conditions (dimness of light)

We use voltage regulator

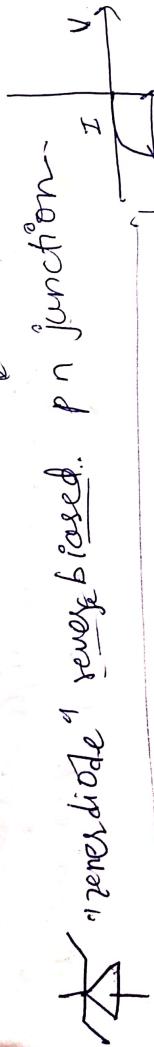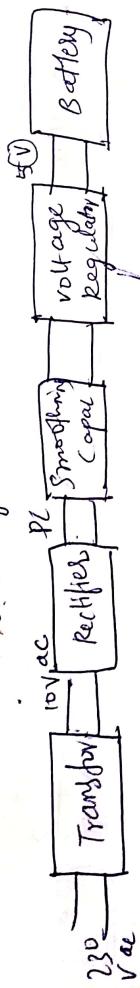

Q) Design a dc power supply to provide 3.7 volts at the output for Indian Supply v.(220V rms) (Full wave rectified).

$$V = 230\sqrt{2} \sin(2\pi \cdot 50 \cdot t)$$

$$= 325 \cdot 2 \sin(\pi t \cdot 50)$$

$$= 100 \cdot 3$$

$$\frac{325 \cdot 2}{N_1} = \frac{100}{N_2}$$

$$\frac{325 \cdot 2}{10} = \frac{100}{N_2}$$

$$N_2 = \frac{1000}{325} \approx 3$$

$$V_o = 9.76V$$

28/01/2020

## Tutorial 1

$V_1 = 200 \sin(2\pi \cdot 50 \cdot t)$   
 $V_2 = 200 \sin(2\pi \cdot 25 \cdot t)$

Find  $V_{avg}$ ,  $V_{rms}$  and plot the graphs

$$\text{① } V_{avg} = \frac{V_m}{\pi} = \frac{200}{\pi} = 63.69 \quad V_{rms} = \frac{200}{\sqrt{2}} = 100$$

$$V_{avg} = \frac{1}{T} \int_{0}^{T/2} 200 \sin(100\pi t) dt = \frac{100}{\pi} \left( -\frac{\cos(100\pi t)}{100\pi} \right) \Big|_0^{\pi/2} = \frac{1}{\pi}$$

$$\text{② } V_{avg} = V_{mg}$$

### ① Half-wave Rectifier

$$\text{a) } V_{avg} = \frac{V_m}{\pi} = \frac{200}{\pi} = 63.69 \quad V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{200}{\sqrt{2}} = 100$$


$$\text{b) } V_{avg} = \frac{V_m}{\pi} = \frac{200}{\pi} = 63.69$$

### ② Full-wave Rectifier.


$$\text{a) } V_{avg} = \frac{2V_m}{\pi} = 2(63.69) \quad V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{200}{\sqrt{2}} = 141.44$$

$$\approx 127.38$$

### Full-wave Rectifier

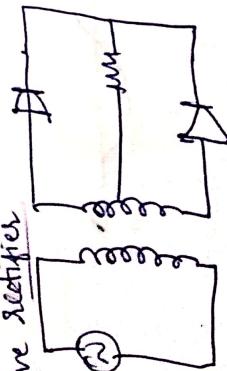

Centre-tapped

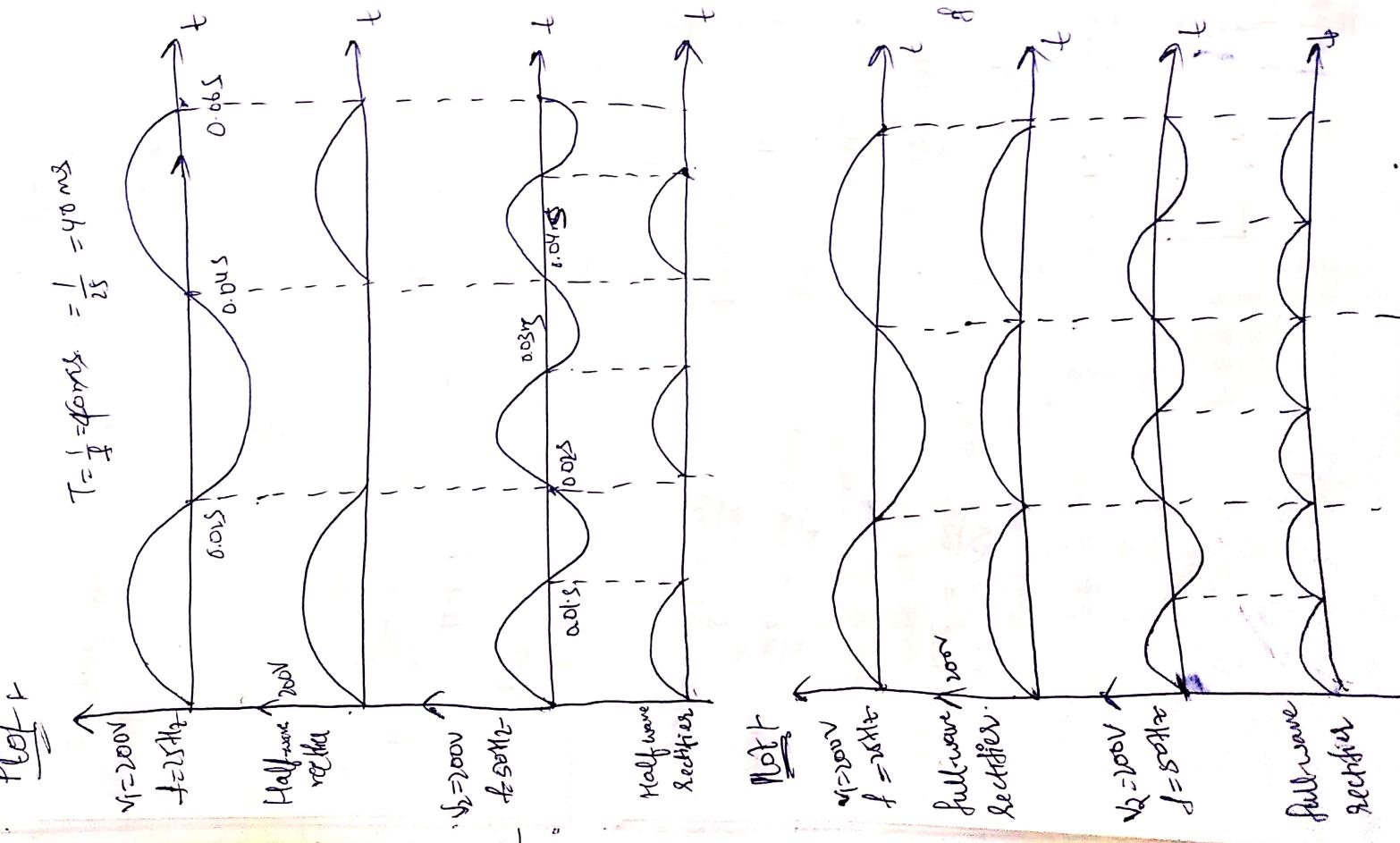

30/01/2020

## Zener Diode Breakdown

In a reverse biased p-n junction the electric field across the junction enables tunneling of electrons from valence band to conduction band of a semi-conductor resulting in large no. of free minority carriers (holes) suddenly reversing current (increases).



Zener breakdown occur at  $V_z > 5V$ .  
Avalanche breakdown at  $V_z > 7V$ .

Avalanche breakdown:

Carriers near the depletion region are accelerated by electric field. These accelerated carriers have sufficient energy to release free electron hole pair through collisions, thereby carrier multiplication occurs resulting in breakdown, called as avalanche breakdown.
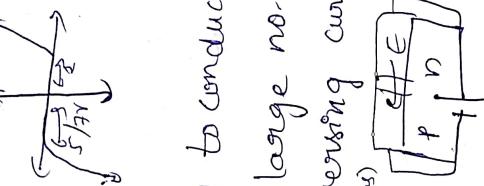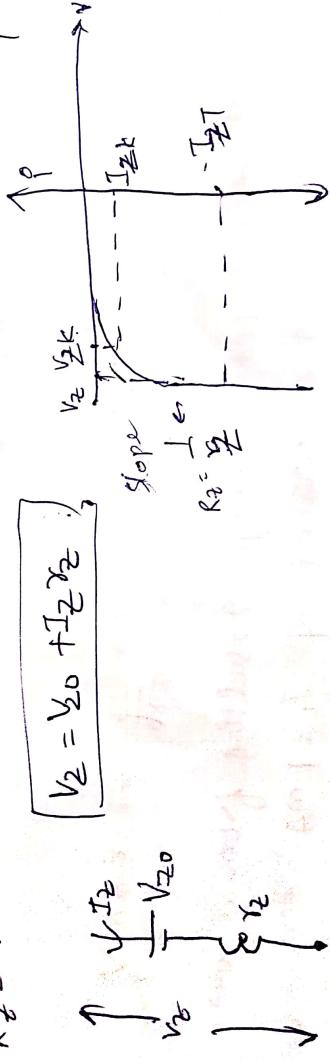
## Modelling Zener diode:

$R_2 = \text{incremental resistance} \Leftrightarrow \text{dynamic resistance}$ .




- Q) A 6.8 V Zener diode in the circuit is specified to have  $V_Z = 6.8V$  at  $I_Z = 5mA$ .  $R_2 = 20\Omega$   $I_{ZK} = 0.2mA$

the supply voltage is normally 10V, and can vary by 1V. (a) Find output voltage  $V_o$  (with load), with

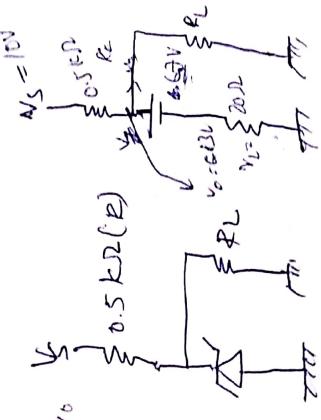(b) find output voltage  $V_o$  at its normal voltage.

$$\begin{aligned}
 V_Z &= V_{Z0} + I_Z R_Z \\
 6.8 - 5 \times 10^{-3} \times 2 \times 10^3 &= V_{Z0} \\
 6.8 - 10^{-1} &= V_{Z0} \\
 6.8 - 0.1 &= V_{Z0} \\
 \boxed{6.7V = V_{Z0}}
 \end{aligned}$$



$$I = \frac{10 - 6.7}{500 + 10} = 6.35A$$

$$\begin{aligned}
 V_o &= 10 - 0.5 \times 6.35mA \\
 V_o &= 6.83V
 \end{aligned}$$

- Q) Find the change in voltage  $V_o$  for change  $\pm 1V_S$ .

### Line regulation

$$\boxed{\Delta V_o = \frac{\Delta V_S \times R_2}{R + R_2}}$$

$$\therefore (\pm 1) \times \frac{20}{500 + 10} = \pm 1 \times \frac{20}{520} = \pm 38.5mV/V_S$$

- Q) Find change in output voltage resulting from a load resistor  $R_L$  that draws a current of  $I_L = 1mA$ . Hence find the load regulation  $= \frac{\Delta V_o}{\Delta I_L}$ .

$$\Delta V_o = V_2 - V_2$$

$$= 20 \times 1 \text{ mA} = -20 \text{ mV/mA}$$

Q3) Find the change in  $V_o$  where  $R_L = 2 \text{ k}\Omega$ .

Sol:-


$\Rightarrow$

(a) Find the value of  $V_i$  when  $K_1 = 0.5 \text{ k}\Omega$

or-

Q4) What is min. value of  $R_L$  for which clamping still operate?

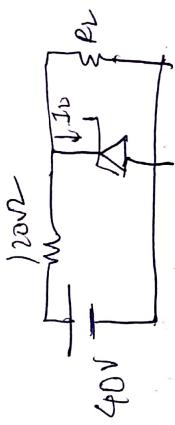- (Q3) Consider Zener diode fig shown in fig. Assume  $V_Z = 12V$ , and  $P_Z = 0$ . a) Calculate the Zener diode current and Power<sub>1</sub> for  $R_L = \infty$ . b) What is value of  $R_L$  such that current in Zener to of the current supplied by 240V source. c) Determine the power dissipated in Zener diode for (b).



Sol:

Transistor

↳ 1.02100

→ Refers to transfer resistance


Two types of transistors:

① Bipolar junction transistor.

② Field Effect transistor.

③

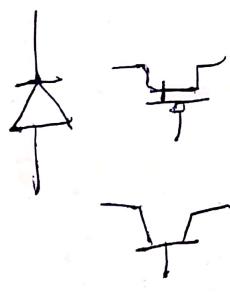- These devices are 3 terminal semi-conductor devices.



BJTR It is a bipolar device (Bipolar Junction Transistor) for the purpose of conduction both the type of carriers (electrons and holes) are used. It is a current controlled device.

→ Compared to a triode, MOSFET, this device is faster and size of BJT is relatively small large compared to a MOSFET!

MOSFET → voltage controlled device.  
One-polar device. For the purpose of conduction either e or  $\text{h}$  alone are used. Terminal

Structural diagrams.



N channel MOSFET.

(PMOS)

Biassing ( Proper amount of input voltage should be given to the corresponding output voltage )

Doping conc' of Emitter:  $10^{19} \text{ cm}^{-3}$   
Base:  $10^{15} \text{ cm}^{-3}$   
Collector:  $10^{17} / \text{cm}^2$

→ Bipolar junction Transistor is not a symmetrical device  
→ Doping conc' of Source & drain regions are same in case of a MOSFET (symmetrical device). *Si or (Insulation)*

MOSFET has all classification of materials.

- the gate terminal is a metal (conductor)
- In between semi-conductor (silicon) and gate terminal there is silicon dioxide ( $\text{SiO}_2$ ) which is insulator.


→ Input resistance of a bipolar transistor (p-n junction) is in the order of few k $\Omega$ s. On the other hand input resistance of a MOSFET is infinitely (Silicon dioxide insulator) in order of Mega ohms ( $1\text{M}\Omega$ )

∴ MOSFET is voltage controlled device.

### Mode of operation of BJT

| <u>Emitter Base J</u> | <u>Collector Base J</u> | <u>Mode</u>                  |
|-----------------------|-------------------------|------------------------------|
| $F_B$                 | $F_B$                   | Saturation (So much current) |
| $F_B$                 | $R_B$                   | Active (Amplifier)           |
| $F_B$                 | $F_B$                   | Cut-off                      |
| $F_B$                 | $F_B$                   | Reverse active.              |

(not in use)  $\times$   $P_B$

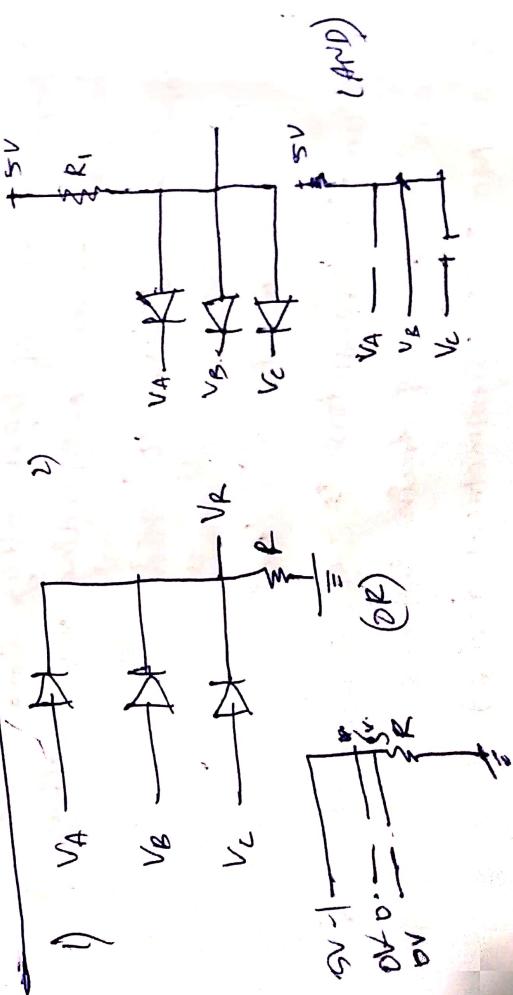

### Ideal Diode Circuit

Assuming that diodes in the circuit of Fig. are ideal, utilize Thévenin's theorem to supply the circuits and thus find the values of the labeled currents and voltages.

(a) Diode is open

10 k $\Omega$  and 10 k $\Omega$  ||


$$10 + R_{eq} = \frac{20}{3}$$

$$R_{eq} = \frac{50}{3} \quad 5 - 10 \left( \frac{50}{3} \right) = 0$$

$$I = 1 \left( \frac{10}{3} \right)$$

$$\boxed{I = 0.333 \text{ mA}}$$
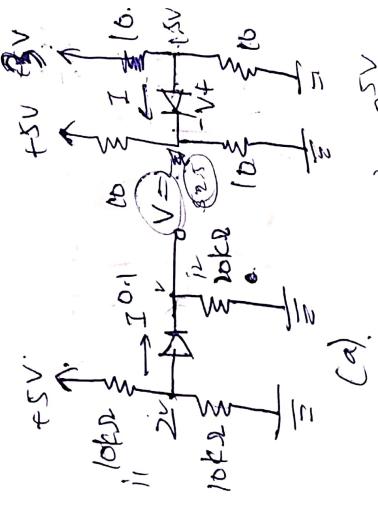
$$5 - 10(0.33) = \boxed{\frac{20}{3} \text{ V}}$$



(a).

(b)

100

5-10

5 - 10 $i - 10j = 0$

$i = 0$

$j = 0$

$V = 5$

$\frac{V-5}{10} + \frac{V-0}{10} = 0$

$V = 2.5$

$i = 2.5$

$j = 2.5$

$V = 2.5$

$\frac{V-5}{10} + \frac{V-0}{10} = 0$

$V = 2.5$

$i = 2.5$

$j = 2.5$

$V = 2.5$

$\frac{V-5}{10} + \frac{V-0}{10} = 0$

$V = 2.5$

$i = 2.5$

$j = 2.5$

$V = 2.5$

$\frac{V-5}{10} + \frac{V-0}{10} = 0$

$V = 2.5$

$i = 2.5$


$j = 2.5$

$V = 2.5$

$\frac{V-5}{10} + \frac{V-0}{10} = 0$

$V = 2.5$

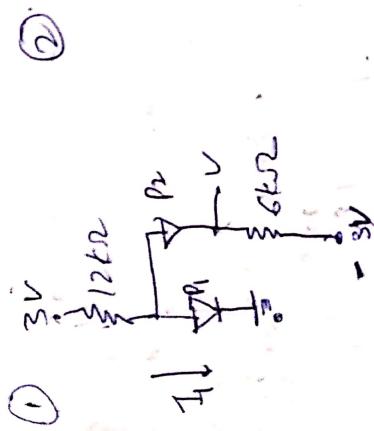- Assuming that diodes in circuits are ideal. Find values of labeled voltage and current.



Terminal char. of diodes  $I = I_s (e^{\frac{V}{nV_T}} - 1)$

$$V_T = 0.0862(273 + T^\circ) \text{ mV} \quad V = \frac{q}{n} \frac{I}{I_s}$$

- After what forward voltage does a diode conduct a current equal to 10,000  $I_s$ ? In terms of  $I_s$ , what current flows in the same diode when its forward voltage is 0.2V?

$$Ans: V = 0.273V$$

- A diode fed with a constant current  $I = 1\text{mA}$  has a voltage  $V = 690\text{ mV}$  at  $20^\circ\text{C}$ . Find the diode voltage at  $-20^\circ\text{C}$  and at  $+85^\circ\text{C}$

$$\text{Soln} \quad V = 0.473\text{mV/C}$$

### Zener Diode Problem

A 9.1V zener diode exhibits its nominal voltage at a test current of  $20\text{mA}$ . At this current the incremental resistance is specified as 10. Find  $V_{Z0}$  of the zener model. Find the zener voltage at a current of  $1\text{mA}$  and at  $50\text{mA}$ .

$$\text{Slt} \quad V_{Z0} = 8.9\text{V} \quad V_2 = 9.0\text{V} (10\text{mA}) \text{ and } V_2 = 9.4 (50\text{mA})$$