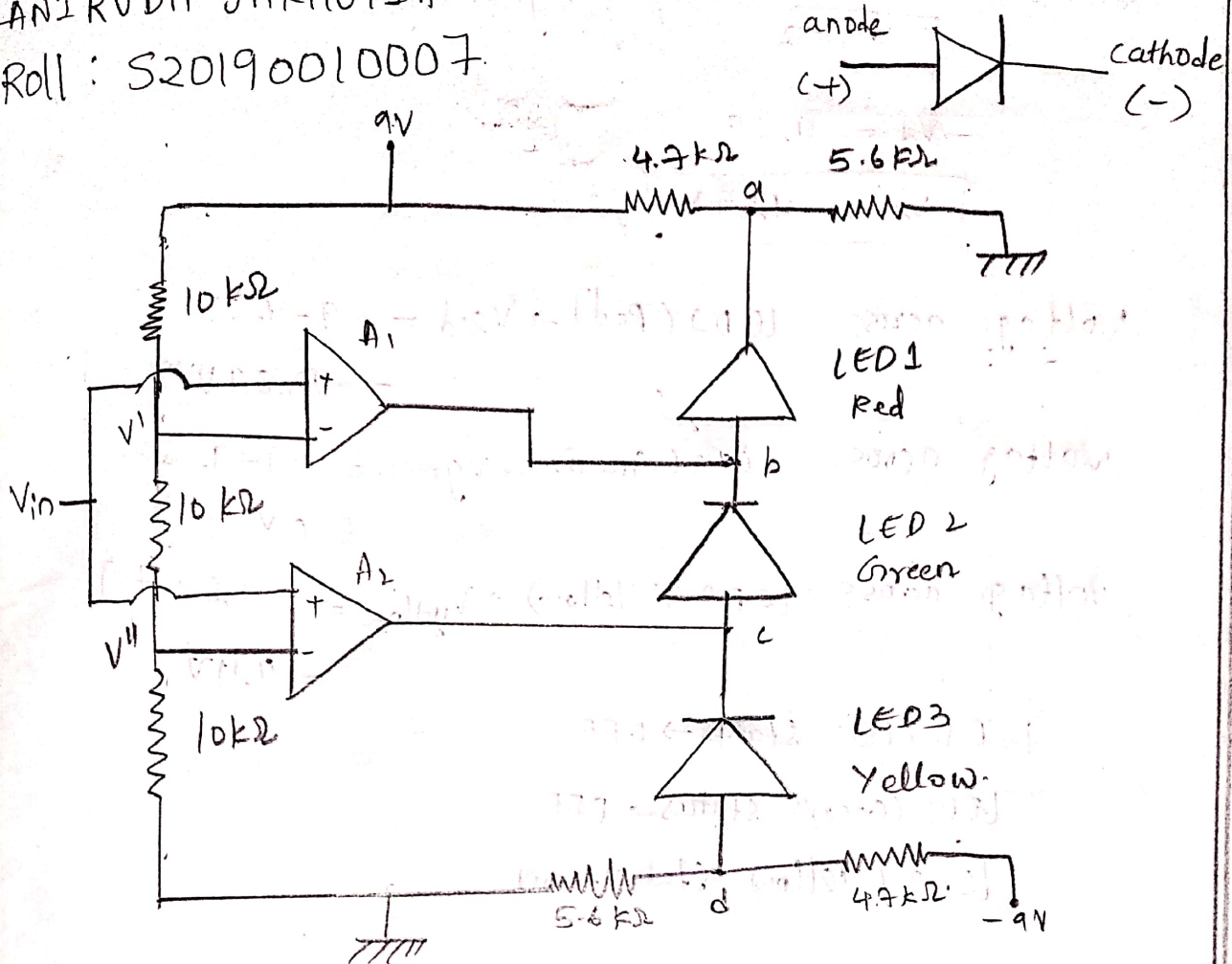


BEC ASSIGNMENT - 1

ANIRUDH JAKHOTIA
Roll : S20190010007



To find V' & V''

We use voltage divider circuit.

$$V' + V'' = 9V$$

$$V'' = \frac{9 \times 10k\Omega}{30k\Omega} = 3V$$

$$V' = 9V - V'' = 9V - 3V = 6V$$

when $V_{in} = 1V$ A_1 output is $-V_{sat} = -9V$ } $\because V_{in} < V_{ref}$
 A_2 output is $-V_{sat} = -9V$

$$V_b = -9V, V_c = -9V$$

$$V_a = \frac{9 \times 5.6k\Omega}{10.3k\Omega} \quad [\because \text{by voltage divider circuit}]$$

$$V_a = 4.89V$$

$$0 - V_d = \frac{(0+9) 5.6k\Omega}{10.3k\Omega}$$

pr' by Voltage divider circuit]

$$-V_d = 4.89$$

$$\boxed{V_d = -4.89V}$$

$$\text{Voltage across LED1 (Red)} \rightarrow V_{red} = -9 - 4.89 \\ = -13.89V$$

$$\text{Voltage across LED2 (Green)} \rightarrow V_{green} = -9 + 9 \\ = 0V$$

$$\text{Voltage across LED3 (Yellow)} \rightarrow V_{yellow} = -4.89 + 9 \\ = 4.11V$$

LED1 (Red) status \rightarrow OFF

LED2 (Green) status \rightarrow OFF

LED3 (Yellow) status \rightarrow ON

When $V_{in} = 5V$

A_1 Output is $-V_{sat} = -9V = V_b$

A_2 Output is $+V_{sat} = +9V = V_c$

$$V_a = 4.89V, \quad V_d = -4.89V$$

$$V_b = -9V, \quad V_c = +9V$$

$$\text{Voltage across LED1 (Red)} = V_{red} = V_b - V_a \\ = -9 - 4.89V \\ = -13.89V$$

$$\text{Voltage across LED2 (Green)} \rightarrow V_{green} = V_c - V_b \\ = 9 + 9 = 18V$$

$$\text{Voltage across LED3 (Yellow)} \rightarrow V_{yellow} = V_d - V_c \\ = -4.89 - 9 \\ = -13.89V$$

LED1 (Red) status \rightarrow OFF

LED2 (green) status \rightarrow ON

LED3 (yellow) status \rightarrow OFF.

When

$$V_{pn} = 7V$$

$$A_1 \text{ Output } P_S + V_{sat} = +9V = V_b$$

$$A_2 \text{ Output is } +V_{sat} = +9V = V_c$$

$$V_a = 4.89V, V_d = -4.89V$$

$$\begin{aligned} \text{Voltage across LED1 (Red)} \quad V_{red} &= V_b - V_a \\ &= 9 - 4.89 \\ &= 4.11V. \end{aligned}$$

$$\begin{aligned} \text{Voltage across LED2 (green)} \quad V_{green} &= V_c - V_b \\ &= 9 - 9 = 0V \end{aligned}$$


$$\begin{aligned} \text{Voltage across LED3 (Yellow)} \quad V_{yellow} &= V_d - V_c \\ &= -4.89 - 9 \\ &= -13.89V \end{aligned}$$

LED1 (Red) status \rightarrow ON


LED2 (green) status \rightarrow OFF

LED3 (yellow) status \rightarrow OFF.

② Zero crossing detector

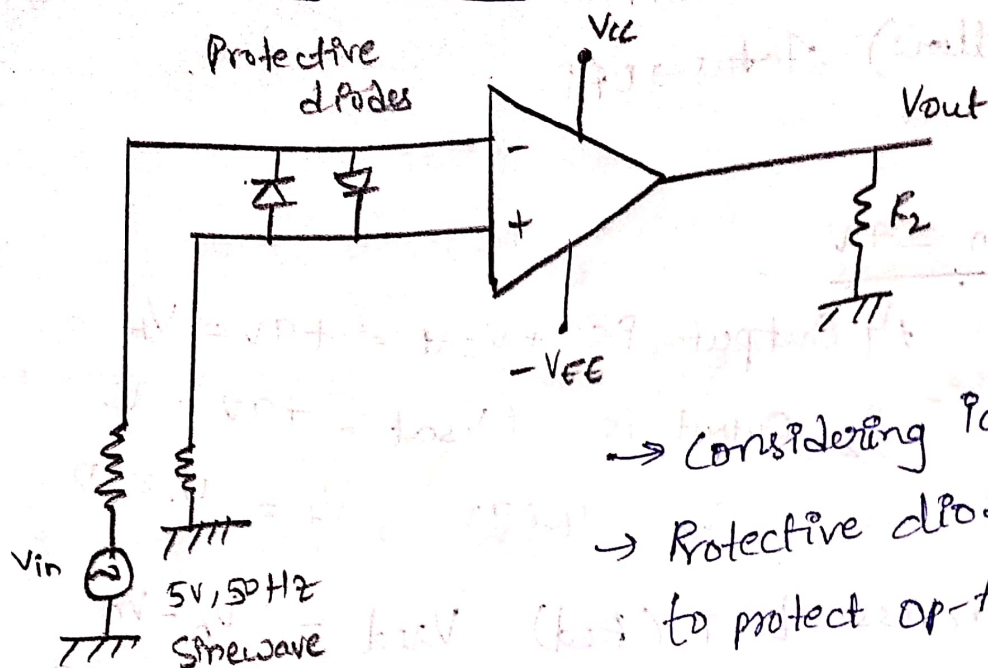

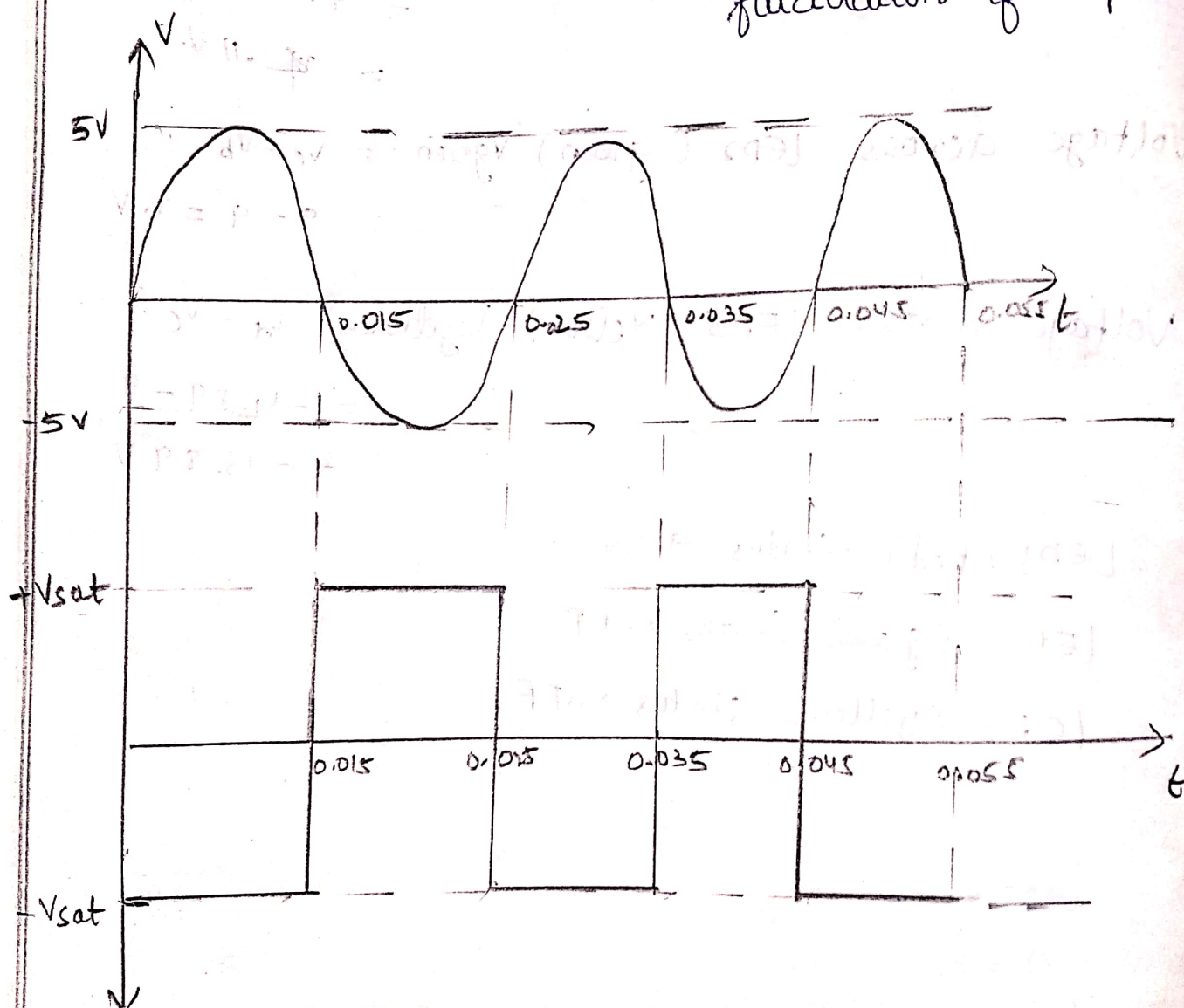→ Considering Ideal diodes;
 → Protective diodes are used to protect op-Amp from fluctuation of Input signal



For every 0.01sec it crosses zero.